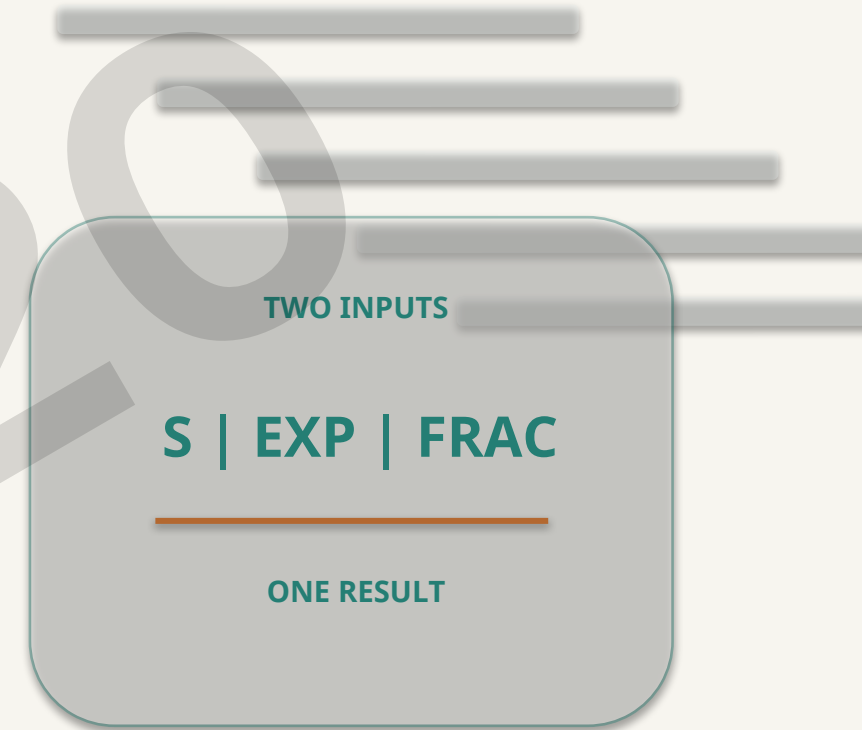


Building a 32-bit Floating-Point Multiplier


Our goal: multiply two floating-point values and pack the answer back into 32 bits.



Made by Sidda, Neeraf, Kanav, Srijan and Md. Sahil

So, what happens after A and B arrive?

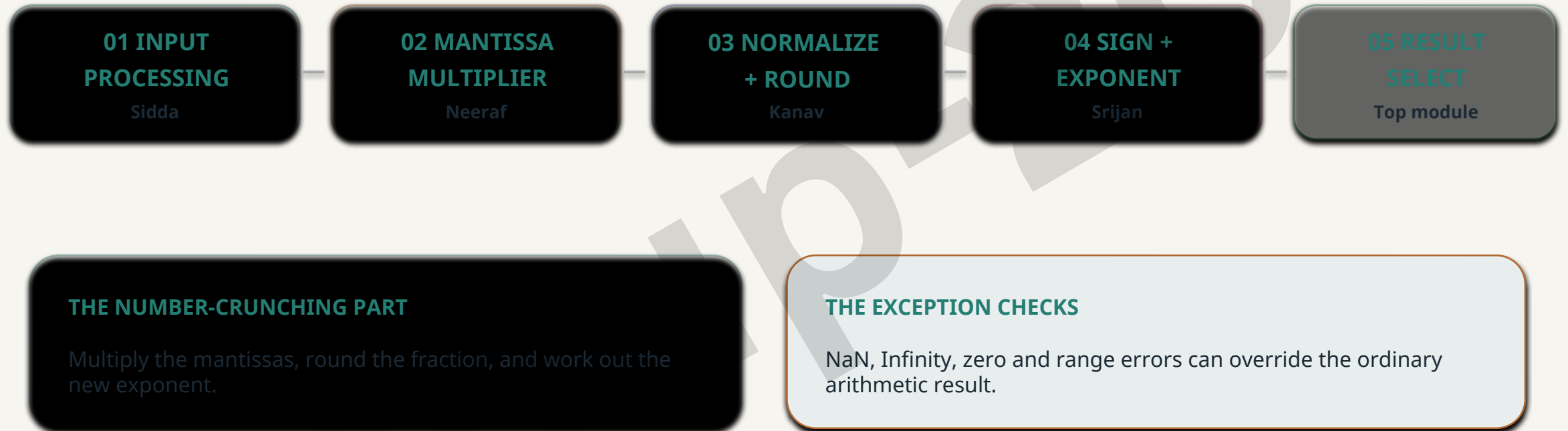
We split the job into smaller modules, then let the top module choose the final 32-bit answer.



The blocks do not all wait in one long chain: the exponent and mantissa paths work from the unpacked inputs, and the top module brings their results together.

A 32-bit float is three fields packed together

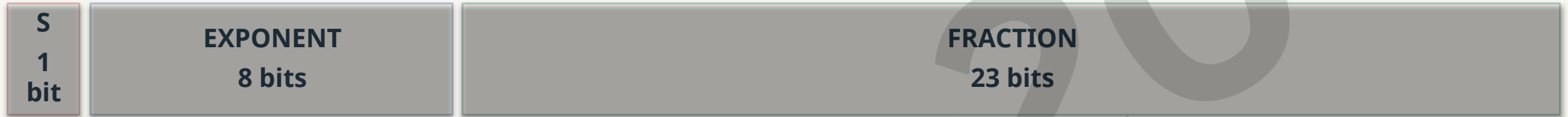Before multiplying anything, we need to know what each group of bits represents.



Sign: 0 = positive
1 = negative

Exponent: stored with bias 127
(unbiased exponent = $E - 127$)

Fraction: precision bits after the
implicit leading bit for normal values

NORMAL VALUE

mantissa = 1.fraction

→ 24-bit internal value

SUBNORMAL VALUE


mantissa = 0.fraction

→ no hidden 1

Exponent 255 marks Infinity or NaN. Exponent 0 is used for zero and subnormal numbers.

make the inputs usable

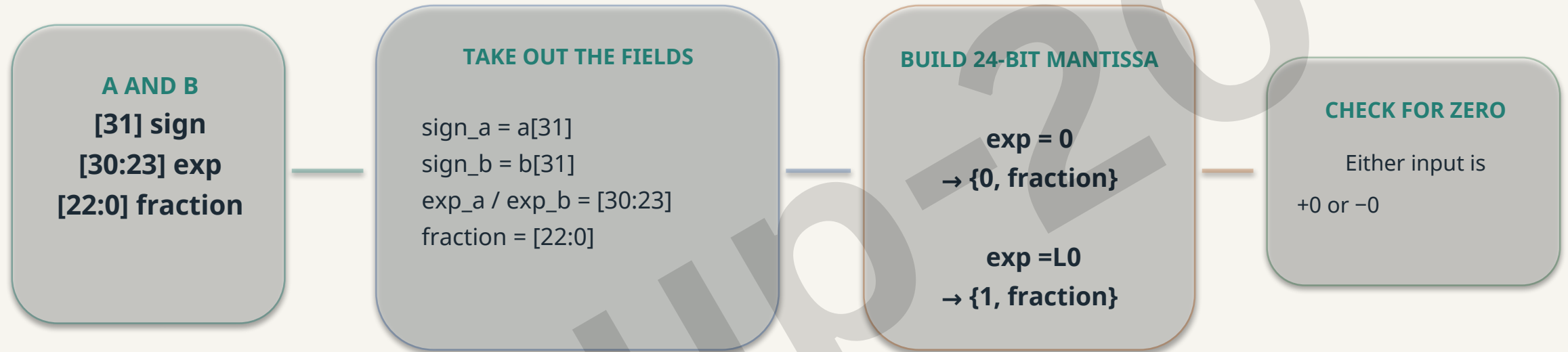Ispliteach32-bitinputintosign,exponentandfraction,buildtheinternalmantissa,and pass along a zero flag.



WHY I KEPTTHISSEPARATE

Other modules receive `sign_a`, `exp_a` and `mant_a` directly. Only normal inputs get the hidden 1.

Small checks here affect the whole calculation

A

FIELDS I PASS ON

Sign is 1 bit
Exponent is 8 bits
Mantissa is 24 bits internally

B

WHEN THE LEADING 1 EXISTS

$\text{exp} = 0 \rightarrow$ add a 0
 $\text{exp} = E0 \rightarrow$ add a 1
This keeps subnormal inputs distinct

C

WHY THE SIGN IS IGNORED

Check $a[30:0]$ and $b[30:0]$
The sign bit is left out, so +0
and -0 both count as zero


D

WHERE NaN / INFINITY ARE CHECKED

This module flags zero. The top module checks $\text{exp} = 255$ and the fraction to tell NaN from Infinity.

Neeraf's part: build the 48-bit product

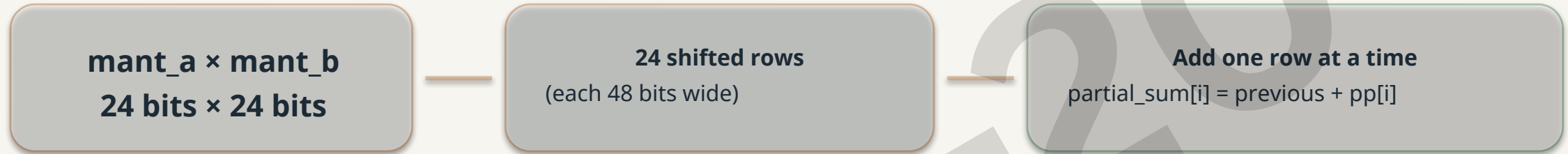For each bit of mant_b, the code makes a shifted row. Those rows are added to get the full product.



WHAT THE SHIFTED ROWS LOOK LIKE




How the adder is built

The 48-bit adder is made from twelve 4-bit CLA blocks. The carry still passes from block to block, but each 4-bit block calculates its internal carries using lookahead logic.

One trade-off: the code is easy to follow, but 23 additions in a row can make the combinational path long.

Kanav's part: line up the product and round it

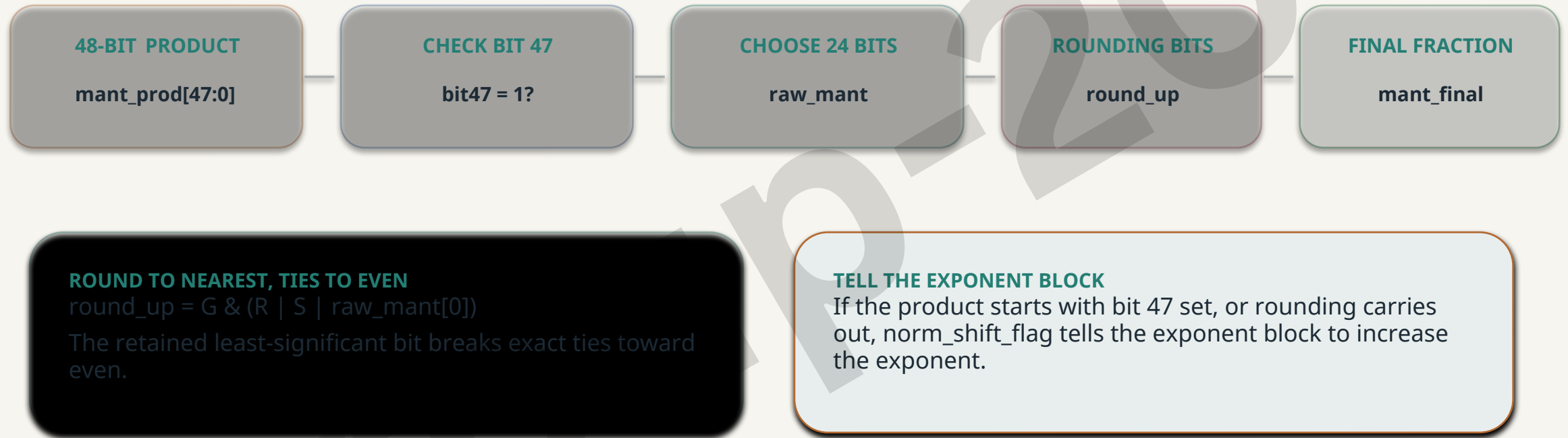Bit47 tells us which 24-bit window to keep. Guard, round and sticky bits then decide whether to add one before dropping the extra bits.



Srijan's part: get the sign and exponent right

The sign is the XOR of the input signs. The exponent block adds the stored exponents, removes one bias, applies the normalization adjustment, and checks the range.

$$\text{sign_out} = \text{sign_a} \text{ XOR } \text{sign_b}$$

$$E_{\text{result}} = E_a + E_b - 127 + \text{norm_shift_flag}$$

1

Add the exponents

$$E_a + E_b$$

2

Subtract the bias

$$-127$$

3

Adjust if needed

$$+ \text{norm_shift_flag}$$

4

Check the result range

underflow / overflow /
final_exp

In this design: overflow becomes Infinity; underflow becomes zero; otherwise, use final_exp.

What if one of the inputs is a special value?

The top module checks these conditions from top to bottom. The first matching branch decides result.

1 If either input is NaN

Return the canonical quiet NaN

2 Infinity multiplied by zero

This case returns NaN

3 Infinity, unless zero was involved

Return signed Infinity

4 Zero input or underflow

Return zero with the calculated sign

5 Overflow

Signed infinity

6 No special case matched

Join sign, exponent and fraction

How we check whether it works

Sahil's testbench tries ten selected cases, waits for the combinational logic to settle, and compares the result bits with the expected pattern.

CASES WE TRY

- 1 Zero $\times$ Infinity $\rightarrow$ NaN
- 2 Zero $\times$ finite $\rightarrow$ Zero
- 3 Infinity $\times$ finite $\rightarrow$ Infinity
- 4 Infinity $\times$ Infinity $\rightarrow$ Infinity
- 5 $1.5 \times 1.5 \rightarrow 2.25$
- 6 $2.0 \times 3.0 \rightarrow 6.0$
- 7 $-2.5 \times 4.0 \rightarrow -10.0$
- 8 RNE rounding increment
- 9 NaN propagation
- 10 Exponent underflow

HOW A TEST PASSES


check_result() waits #1, compares the 32-bit values, and updates the pass count. For NaN, it accepts any result with an all-ones exponent and a nonzero fraction.

LOOK INSIDE WITH A WAVEFORM

The testbench writes dump.vcd. Opening it in a waveform viewer lets us follow signals and see where a result came from.

Putting the whole design together

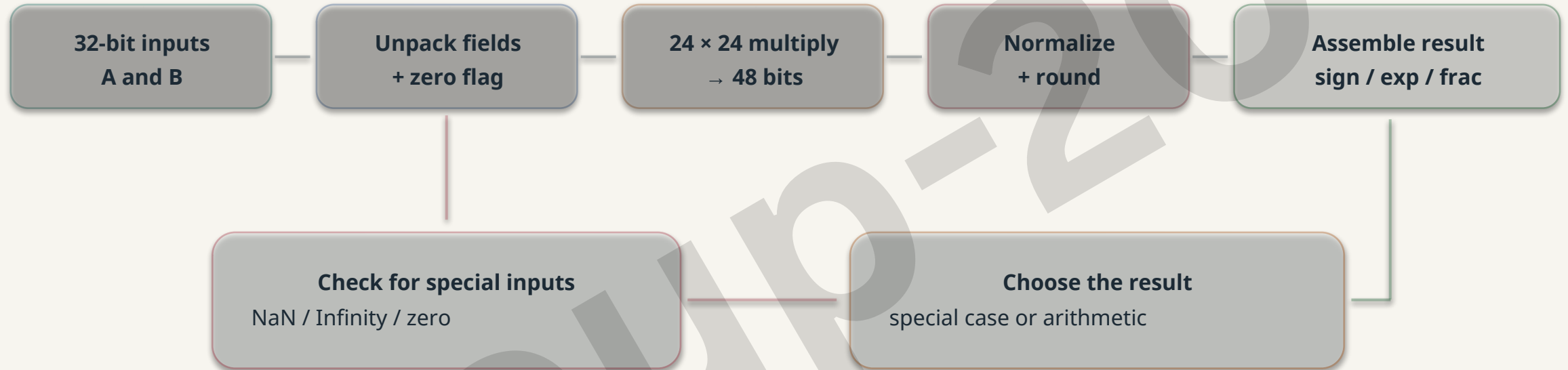The mantissa and exponent paths calculate their parts, while the top module handles special cases and assembles the final word.



At the end: a 32-bit output, a test summary, and a VCD file we can inspect when something goes wrong.

What is working—and what still needs attention

The current code gives us a modular starting point, but it is worth being precise about its limits.

WHAT IS IN PLACE

- Each major job has its own module
- The same CLA structure is reused in several places
- Special results are handled in a clear priority order
- The testbench covers normal and special cases

CURRENT LIMITS

- The partial products are added one after another
- Subnormal results are not fully supported; underflow is flushed to zero
- Only selected test cases are included so far
- No randomized comparison against a reference is included

WHAT WE WOULD TRY NEXT

- Support gradual underflow if full IEEE-754 behavior is required
- Test negative zero and swap A/B in test cases
- Compare many random inputs with a trusted software result
- Check hardware area and timing after synthesis

Who worked on which block?

This split follows the ownership comments and module names in our source files.

Sidda	input_processing	Splits the input fields, builds 24-bit mantissas and flags zero operands.
Neeraf	mantissa_multiplier	Makes the shifted partial-product rows and adds them into a 48-bit product.
Kanav	normalization_unit& rounding	Chooses the product bits to keep and applies guard/round/sticky rounding.
Srijan	sign_exponent_unit	Works out the result sign and exponent, then flags overflow or underflow.
Md. Sahil	tb_fp_multiplier	Runs ten selected tests, checks expected outputs, and creates the VCD waveform.